


## Series and Parallel Circuits




**Series**

**Parallel**


<b>Equivalent Resistance</b>		
<b>Current</b>		
<b>Voltage</b>		
<b>Circuit</b>		

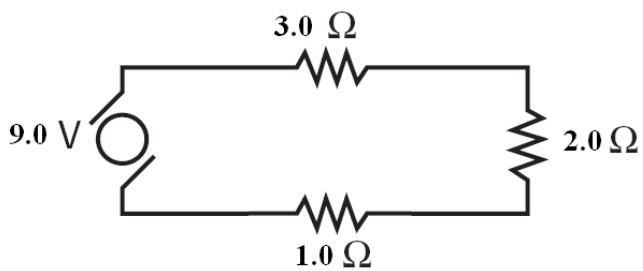

$R_T$	$I_T$	$V_T$	$P_T$
$R_1$	$I_1$	$V_1$	$P_1$
$R_2$	$I_2$	$V_2$	$P_2$
$R_3$	$I_3$	$V_3$	$P_3$

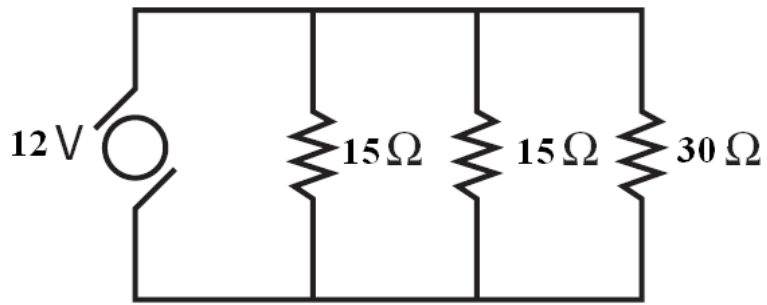

$R_T$	$I_T$	$V_T$	$P_T$
$R_1$	$I_1$	$V_1$	$P_1$
$R_2$	$I_2$	$V_2$	$P_2$
$R_3$	$I_3$	$V_3$	$P_3$

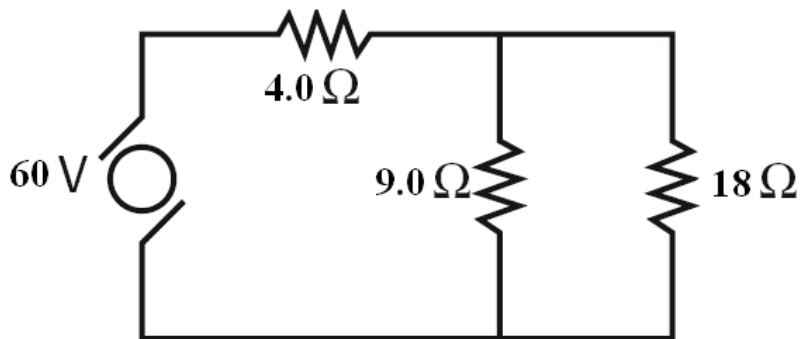

$R_T$	$I_T$	$V_T$	$P_T$
$R_1$	$I_1$	$V_1$	$P_1$
$R_2$	$I_2$	$V_2$	$P_2$
$R_3$	$I_3$	$V_3$	$P_3$